

Tutorial - 2

RF & Microwave Theory
(EC31005)

1. A two-port network is driven at both ports such that the port voltage and currents have the following values ($Z_0 = 50 \Omega$)

$$V_1 = 10\angle 90^\circ, \quad I_1 = 0.2\angle 90^\circ$$

$$V_2 = 8\angle 0^\circ, \quad I_2 = 0.16\angle -90^\circ.$$

Determine the input impedance seen at each port, and find the incident and reflected voltage at each port.

Given that $V_1 = 10\angle 90^\circ$, $I_1 = 0.2\angle 90^\circ$ and $V_2 = 8\angle 0^\circ$, $I_2 = 0.16\angle -90^\circ$.

The input impedance seen at port 1,

$$Z_{in(1)} = \frac{V_1}{I_1} = \frac{10\angle 90^\circ}{0.2\angle 90^\circ} = 50 \Omega.$$

And input impedance seen at port 2,

$$Z_{in(2)} = \frac{V_2}{I_2} = \frac{8\angle 0^\circ}{0.16\angle -90^\circ} = 50\angle 90^\circ = (0 + j50) \Omega.$$

As the incident and reflected voltage at port (n) is given by,

$$V_n^+ = \frac{(V_n + Z_0 I_n)}{2} \quad \text{and} \quad V_n^- = \frac{(V_n - Z_0 I_n)}{2} \dots \dots \dots (i)$$

contd.

So incident voltage at port 1,

$$V_1^+ = \frac{(10\angle 90^\circ + 50 * 0.2\angle 90^\circ)}{2} = \frac{j10 + j10}{2} = j10 = 10\angle 90^\circ$$

And the reflected Voltage At Port 1,

$$V_1^- = \frac{(10\angle 90^\circ - 50 * 0.2\angle 90^\circ)}{2} = 0$$


Now The Incident Voltage At Port 2,

$$V_2^+ = \frac{(8\angle 0^\circ + 50 * 0.16\angle -90^\circ)}{2} = \frac{8 - j8}{2} = 5.65\angle -45^\circ$$

And hence the reflected voltage at port 2,

$$V_2^- = \frac{(8\angle 0^\circ - 50 * 0.16\angle -90^\circ)}{2} = \frac{8 + j8}{2} = 5.65\angle 45^\circ$$

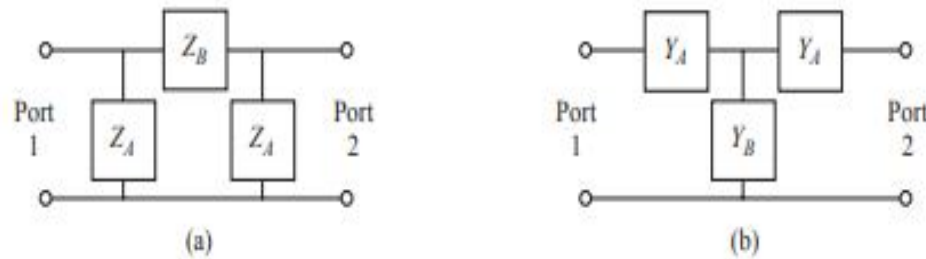2. Derive the [Z] and [Y] matrices for the two-port networks shown in the figure below



If we have voltage and current at port 1 and port 2 is (V_1, I_1) and (V_2, I_2) respectively, then from the two port network, applying KVL and KCL,

$$Z_{11} = \frac{V_1}{I_1} (\text{given } I_2 = 0) = \frac{V_1}{V_1 \left(\frac{2Z_A + Z_B}{Z_A(Z_A + Z_B)} \right)} = \frac{Z_A(Z_A + Z_B)}{2Z_A + Z_B} = Z_{22} \quad (\text{By Symmetry})$$

$$Z_{21} = \frac{V_2}{I_1} (\text{given } I_2 = 0) = \frac{I_1 Z_{11} \left(\frac{Z_A}{Z_A + Z_B} \right)}{I_1} = \frac{Z_A^2}{2Z_A + Z_B} = Z_{12} \quad (\text{By Symmetry})$$

$$Y_{11} = \frac{I_1}{V_1} (\text{given } V_2 = 0) = \frac{I_1}{I_1 \left(\frac{Z_A Z_B}{Z_A + Z_B} \right)} = \frac{Z_A + Z_B}{Z_A Z_B} = Y_{22} \quad (\text{By Symmetry})$$

Contd.

$$Y_{21} = \frac{I_2}{V_1} \text{ (given } V_2 = 0) = \frac{-V_1}{Z_B V_1} = \frac{-1}{Z_B} = Y_{22} \text{ (By Symmetry)}$$

(b) If we have voltage and current at port 1 and port 2 are (V_1, I_1) and (V_2, I_2) respectively, then from the two port network, applying KVL and KCL,

$$Z_{11} = \frac{V_1}{I_1} \text{ (given } I_2 = 0) = \frac{(Y_A + Y_B)}{Y_A Y_B} = Z_{22} \text{ (By Symmetry)}$$

$$Z_{21} = \frac{V_2}{I_1} \text{ (given } I_2 = 0) = \frac{-1}{Y_B} = Z_{12} \text{ (By Symmetry)}$$

$$Y_{11} = \frac{I_1}{V_1} \text{ (given } V_2 = 0) = \frac{Y_A(Y_A + Y_B)}{2Y_A + Y_B} = Y_{22} \text{ (By Symmetry)}$$

$$Y_{21} = \frac{I_2}{V_1} \text{ (given } V_2 = 0) = \frac{Y_A^2}{2Y_A + Y_B} = Y_{22} \text{ (By Symmetry)}$$

3. Consider a lossless air-filled rectangular waveguide with dimensions $a = 22.86$ mm and $b = 10.16$ mm. Calculate the value of the propagation constant (per meter) of the corresponding propagation mode at 10 GHz operating frequency.

Ans: $a = 22.86$ mm, $b = 10.16$ mm, frequency = 10 GHz

Assume dominant mode of propagation in the waveguide i.e. TE₁₀ mode.

$m = 1$ and $n = 0$

Cut off frequency for TE₁₀ mode is given by

$$f_c = \frac{c}{2} \sqrt{\left(\frac{m}{a}\right)^2 + \left(\frac{n}{b}\right)^2} = \frac{c}{2a} = \frac{3 \times 10^{10}}{2 \times 2.286} = 6.56 \text{ GHz}$$

Since cut off frequency is 6.56 GHz, the frequency of 10 GHz will propagate in the waveguide.

Propagation constant $\gamma = \alpha + j\beta$

Since the waveguide is lossless, $\alpha = 0$, β is phase constant

$$\begin{aligned} \beta &= \frac{2\pi}{\lambda_g} = \frac{2\pi}{\lambda_0 / \sqrt{1 - \left(\frac{\lambda_0}{\lambda_c}\right)^2}} = \frac{2\pi f}{c} \sqrt{1 - \left(\frac{f_c}{f}\right)^2} \\ &= \frac{2\pi \cdot 10 \times 10^9}{3 \times 10^8} \sqrt{1 - \left(\frac{6.56}{10}\right)^2} = \mathbf{158 \text{ rad.m}^{-1}} \end{aligned}$$

4. An air – filled rectangular waveguide of cross sectional dimension $a \times b$ ($a > b$) has a cut off frequency of 6 GHz for the dominant TE₁₀ mode. If the cutoff frequency of the TM₁₁ mode is 15 GHz, calculate the cut off frequency of the TE₀₁ mode

Ans: Cut off frequency $f_c = 6\text{GHz}$ for dominant mode

For dominant mode cut off wavelength $\lambda_c = 2a$

$$\lambda_{c10} = \frac{c}{f_{c10}} = \frac{3 \times 10^{10}}{6 \times 10^9} = 5\text{cm} = 2a$$

$$a = 2.5\text{cm}$$

f_c for TM₁₁ mode is 15GHz

$$f_c = \frac{c}{2} \sqrt{\left(\frac{1}{a}\right)^2 + \left(\frac{1}{b}\right)^2} = 15 \times 10^9$$


$$b = \frac{2.5}{\sqrt{5.25}}$$

$$f_c \text{ for TE}_{01} \text{ mode} = \frac{c}{2b} = \frac{3 \times 10^{10}}{2.5} \sqrt{5.25} = \mathbf{13.75\text{GHz}}$$

5. Consider two two-port networks with individual scattering matrices $[S^A]$ and $[S^B]$. Show that the overall S_{21} parameter of the cascade of these networks is given by:

$$S_{21} = \frac{S_{21}^A S_{21}^B}{1 - S_{22}^A S_{11}^B}$$


Considering wave amplitude as shown,

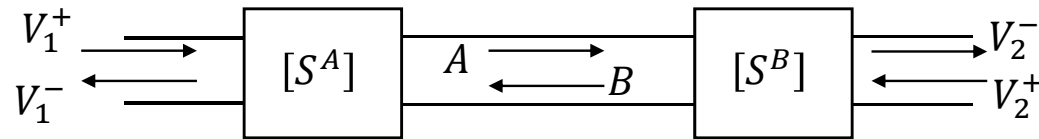

Then,

$$\begin{bmatrix} V_1^- \\ A \end{bmatrix} = [S^A] \begin{bmatrix} V_1^+ \\ B \end{bmatrix} \quad \begin{bmatrix} B \\ V_2^- \end{bmatrix} = [S^B] \begin{bmatrix} A \\ V_2^+ \end{bmatrix} \quad \begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = [S] \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix} \quad S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+=0}$$

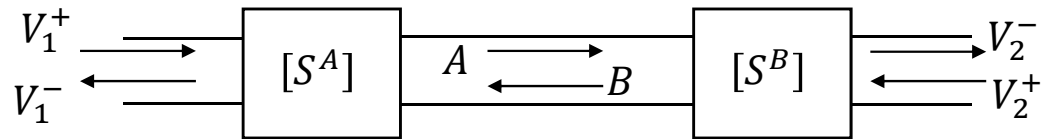So, we have $B = S_{11}^B A$, and $V_2^- = S_{21}^B A$



$$A = S_{21}^A V_1^+ + S_{22}^A B = S_{21}^A V_1^+ + S_{22}^A S_{11}^B A$$

Putting the value of A, we get,

$$\frac{V_2^-}{S_{21}^B} = S_{21}^A V_1^+ + S_{22}^A S_{11}^B \frac{V_2^-}{S_{21}^B}$$

So,

$$S_{21} = \frac{S_{21}^A S_{21}^B}{1 - S_{22}^A S_{11}^B}$$

6. A four-port network has the scattering matrix shown as follows.

(a) Is this network lossless?

(b) Is this network reciprocal?

(c) What is the return loss at port 1 when all other ports are terminated with matched loads?

(d) What is the insertion loss and phase delay between ports 2 and 4 when all other ports are terminated with matched loads?

(e) What is the reflection coefficient seen at port 1 if a short circuit is placed at the terminal plane of port 3 and all other ports are terminated with matched loads?

$$[S] = \begin{bmatrix} 0.178\angle 90^\circ & 0.6\angle 45^\circ & 0.4\angle 45^\circ & 0 \\ 0.6\angle 45^\circ & 0 & 0 & 0.3\angle -45^\circ \\ 0.4\angle 45^\circ & 0 & 0 & 0.5\angle -45^\circ \\ 0 & 0.3\angle -45^\circ & 0.5\angle -45^\circ & 0 \end{bmatrix}.$$

(a) To be lossless, $[S]$ must be unitary. From 1st row:

$$|S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 + |S_{14}|^2 = 0.552 \neq 1 \quad \Rightarrow \text{So, NOT lossless.}$$

(b) The $[S]$ matrix is symmetric, so it is reciprocal.

(c) When ports 2, 3, 4 are matched,

$$\text{So, } RL = -20 \log |\Gamma| = -20 \log(0.178) = 15 \text{ dB}$$

(d) For ports 1 and 3 terminated with Z_0 , we have

$$V_1^+ = 0, V_3^+ = 0, \text{ So, } V_4^- = S_{42} V_2^+$$

$$IL = -20 \log |S_{42}| = -20 \log(0.3) = 10.5 \text{ dB}$$

$$\text{phase delay} = +45^\circ$$

(e) For a short at port 3, Z_0 on the other ports, we have

$$V_2^+ = V_4^+ = 0$$

$$V_3^+ = -V_3^-$$

$$V_1^- = S_{11} V_1^+ + S_{13} V_3^+ = S_{11} V_1^+ - S_{13} V_3^-$$

$$V_3^- = S_{31} V_1^+$$

Then,

$$\Gamma = \frac{V_1^-}{V_1^+} = S_{11} - S_{13} S_{31} = 0.178j - (0.4 \angle 45^\circ)(0.4 \angle 45^\circ) = 0.178j - 0.16j = 0.018j =$$

$$0.018 \angle 90^\circ$$

7. A transmission line resonator is fabricated from a $\lambda/4$ length of open-circuited line. Find the unloaded Q of this resonator if the complex propagation constant of the line is $\alpha + j\beta$.

Ans. Unloaded Q as Q_0 , Input Impedance as Z_{in}

$$l = \lambda / 4 = \frac{\pi v_p}{2\omega_0}$$

$$\text{at } \omega = \omega_0 \quad \beta l = \frac{\omega_0 l}{v_p} + \frac{\Delta\omega l}{v_p} = \frac{\pi}{2} \left(1 + \frac{\Delta\omega}{\omega_0}\right)$$

$$\tan \beta l = -\cot\left(\frac{\Delta\omega\pi}{2\omega_0}\right) = -\frac{2\omega_0}{\Delta\omega\pi}$$


$$\tanh \alpha l = \alpha l$$

$$Z_{in} = Z_0 \frac{1 + j \tan \beta l \tanh \alpha l}{\tanh \alpha l + j \tan \beta l} = Z_0 \frac{1 - j \frac{2\omega_0}{\Delta\omega\pi} \alpha l}{\alpha l - j \frac{2\omega_0}{\Delta\omega\pi}} = Z_0 \left(\alpha l + j \frac{\Delta\omega\pi}{2\omega_0} \right) = R + 2jL\Delta\omega$$


$$R = Z_0 \alpha l, L = \frac{\pi Z_0}{4\omega_0}$$

$$Q_0 = \frac{\omega_0 L}{R} = \frac{\pi}{4\alpha l} = \frac{\beta}{2\alpha}$$

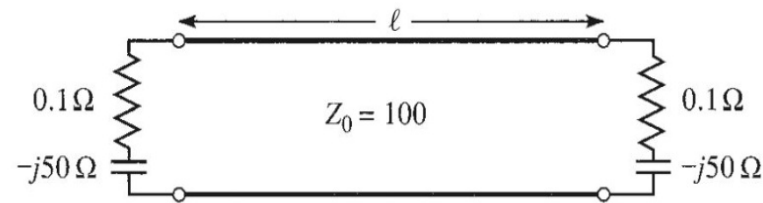8. A transmission line resonator is made from a length ℓ of lossless transmission line of characteristic impedance $Z_0 = 100 \Omega$. If the line is terminated at both ends as shown below, find ℓ/λ for the first resonance, and the unloaded Q of this resonator.



Ans.

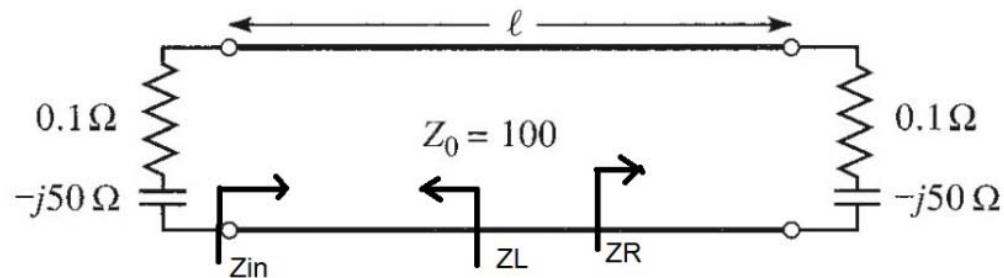

Since the resonator is symmetrical, at midpoint of line we must have, $Z_L = Z_R^* = Z_R$
 Let $t = \tan \beta \ell / 2$ and $Z_L = R_L + jX_L$, ($R_L = 0.1$, $X_L = -50$)

$$Z_R = Z_0 \frac{Z_L + jZ_0 t}{Z_0 + jZ_L t} = Z_0 \frac{R_L + j(Z_L t + X_L)}{(Z_0 - X_L t) + jR_L t}$$

$$\text{Im}\{Z_R\} = 0 \Rightarrow (X_L + Z_o t)(Z_o + X_L t) - R_L^2 t = 0$$

$$t = -0.75 \pm 1.25$$

$$\beta l = 53.1^\circ$$

So,
$$l = \frac{53.1^\circ}{360^\circ} \lambda = 0.1475 \lambda$$

$$\therefore l / \lambda = 0.1475$$

$$\tan \beta l = 1.332$$

$$Z_{in} = Z_o \frac{Z_L + jZ_o \tan \beta l}{Z_o + jZ_L \tan \beta l} = 100 \frac{(.1 - j50) + j133.2}{100 + j(0.1 - j50)1.332} = 0.1 + j50 \Omega$$

$$Q_0 = \frac{\omega_0 L}{R} = \frac{X_L}{R} = 50 / 0.2 = 250$$

